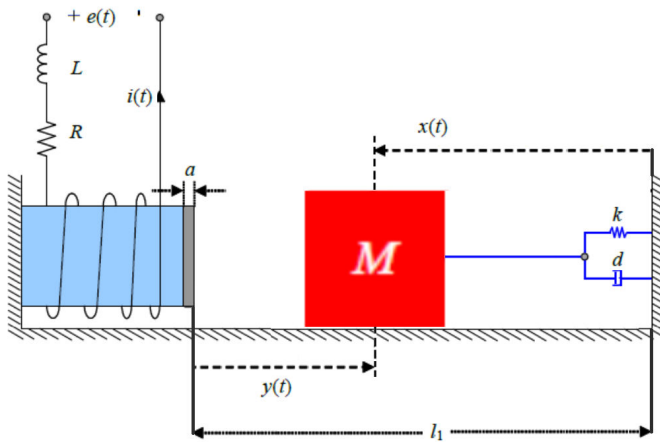


Solución Tarea N°1

```
clear all, close all
format shortG
set(0, 'DefaultAxesFontName', 'Times New Roman')
set(0, 'DefaultAxesFontSize', 11)
set(0, 'DefaultLineLineWidth', 2)
set(0, 'DefaultAxesFontWeight', 'bold')
```

Problema 1: Estudiar un sistema electromecánico.



a) Modelo.

$$M \frac{d^2}{dt^2} x(t) = F_m(t) - k(x(t) - l_0) - d \frac{d}{dt} x(t), \quad e(t) = L \frac{d}{dt} i(t) + Ri(t).$$

$$M \frac{d^2}{dt^2} x(t) = \frac{k i(t)^2}{y(t) + a} - k(x(t) - l_0) - d \frac{d}{dt} x(t), \quad e(t) = L \frac{d}{dt} i(t) + Ri(t).$$

$$M \frac{d^2}{dt^2} x(t) = \frac{k i(t)^2}{l_1 - x(t) + a} - k(x(t) - l_0) - d \frac{d}{dt} x(t), \quad e(t) = L \frac{d}{dt} i(t) + Ri(t).$$

Clasificación de cantidades.

Orden: 3

Parametros: $M, k, d, k_i, l_0, l_1, a, R, L$.

Entradas: $e(t)$

Perturbaciones: no hay

Salidas: $x(t)$

Variables de estado: $x_1(t) = x(t), \quad x_2(t) = \frac{d}{dt}x(t), \quad x_3(t) = i(t)$.

Ecuaciones de estado.

$$u(t) = e(t).$$

$$\frac{d}{dt}x_1(t) = x_2(t),$$

$$\frac{d}{dt}x_2(t) = \frac{1}{M} \frac{k_i x_3(t)^2}{l_1 - x_1(t) + a} - \frac{k}{M} (x_1(t) - l_0) - \frac{d}{M} x_2(t),$$

$$\frac{d}{dt}x_3(t) = \frac{1}{L} u(t) - \frac{R}{L} x_3(t).$$

b) Clasificación del sistema.

No lineal

Continuo

Dinámico

Causal

Tiempo invariante

Parametros concentrados

c) Punto de operación.

$$0 = x_{2o},$$

$$0 = \frac{1}{M} \frac{k_i x_{3o}^2}{l_1 - x_{1o} + a} - \frac{k}{M} (x_{1o} - l_0) - \frac{d}{M} x_{2o},$$

$$0 = \frac{1}{L} u_o - \frac{R}{L} x_{3o}.$$

```
syms M k d ki l0 l1 a R L
syms x10 x20 x30 u0
% Ecuaciones en el punto de op.
eq1 = 0 == x20;
eq2 = 0 == (1/M)*ki*x30^2/(l1 - x10 + a) - k/M*(x10 - l0) - d/M*x20;
eq3 = 0 == 1/L*u0 - R/L*x30;
% Utiliza ecuación arbitraria para que n° ecuacion = n° incognitas.
eq4 = u0 == 2;
S = solve([eq1 eq2 eq3 eq4],[x10 x20 x30 u0])
```

```
S = struct with fields:
  x10: [2×1 sym]
  x20: [2×1 sym]
  x30: [2×1 sym]
  u0: [2×1 sym]
```

```
S.x10, S.x20, S.x30, S.u0
```

```
ans =
```

$$\begin{pmatrix} \frac{R a + R l_0 + R l_1 + \sigma_1}{2 R} \\ \frac{R a + R l_0 + R l_1 - \sigma_1}{2 R} \end{pmatrix}$$

where

$$\sigma_1 = \sqrt{\frac{k R^2 a^2 - 2 k R^2 a l_0 + 2 k R^2 a l_1 + k R^2 l_0^2 - 2 k R^2 l_0 l_1 + k R^2 l_1^2 - 16 k i}{k}}$$

ans =

$$\begin{pmatrix} 0 \\ 0 \end{pmatrix}$$

ans =

$$\begin{pmatrix} \frac{2}{R} \\ \frac{2}{R} \end{pmatrix}$$

ans =

$$\begin{pmatrix} 2 \\ 2 \end{pmatrix}$$

Linealización.

```
dx1 = x20;
dx2 = (1/M)*ki*x30^2/(l1 - x10 + a) - k/M*(x10 - l0) - d/M*x20;
dx3 = 1/L*u0 - R/L*x30;
A = [diff(dx1,x10) diff(dx1,x20) diff(dx1,x30);
     diff(dx2,x10) diff(dx2,x20) diff(dx2,x30);
     diff(dx3,x10) diff(dx3,x20) diff(dx3,x30)]
```

A =

$$\begin{pmatrix} 0 & 1 & 0 \\ \frac{k_i x_{30}^2}{M(a+l_1-x_{10})^2} - \frac{k}{M} & -\frac{d}{M} & \frac{2k_i x_{30}}{M(a+l_1-x_{10})} \\ 0 & 0 & -\frac{R}{L} \end{pmatrix}$$

```
b = [diff(dx1,u0) diff(dx2,u0) diff(dx3,u0)]'
```

b =

$$\begin{pmatrix} 0 \\ 0 \\ \frac{1}{L} \end{pmatrix}$$

$$\frac{d}{dt} \Delta \mathbf{x}(t) = \frac{d}{dt} \begin{bmatrix} x_1(t) - x_{1o} \\ x_2(t) - x_{2o} \\ x_3(t) - x_{3o} \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ \frac{k_i x_{3o}^2}{M(a+l_1-x_{1o})^2} - \frac{k}{M} & -\frac{d}{M} & \frac{2k_i x_{3o}}{M(a+l_1-x_{1o})} \\ 0 & 0 & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} x_1(t) - x_{1o} \\ x_2(t) - x_{2o} \\ x_3(t) - x_{3o} \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ \frac{1}{L} \end{bmatrix} (u(t) - u_0)$$

$$\Delta y(t) = y(t) - y_0 = \begin{bmatrix} 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} x_1(t) - x_{1o} \\ x_2(t) - x_{2o} \\ x_3(t) - x_{3o} \end{bmatrix}$$

c) Simulación sistema linealizado

```
% Parametros
```

```
R = 0.5;
```

```
L = 50e-3;
```

```
a = 2e-2;
```

```
ki = 3e-3;
```

```
l1 = 50e-2;
```

```
l0 = 30e-2;
```

```
M = 250e-3;
```

```
k = 24.5;
```

```
d = 1.5;
```

% Punto de op.

```
p_operacion = eval([S.x10 S.x20 S.x30 S.u0])
```

```
p_operacion = 2x4
```

```
    0.5107    0    4    2  
    0.3093    0    4    2
```

% hay 2 puntos.. se escoge uno arbitrario.

```
x10 = p_operacion(2,1); x20 = p_operacion(2,2); x30 = p_operacion(2,3); u0 = p_operacion(2,4);
```

```
A = eval(A), b = eval(b), c = [1 0 0]
```

```
A = 3x3
```

```
    0    1    0  
 -93.675  -6  0.45562  
    0    0   -10
```

```
b = 3x1
```

```
    0  
    0  
   20
```

```
c = 1x3
```

```
    1    0    0
```

% Definición del sistema linealizado

```
iman_lineal = ss(A,b,c,0);
```

% Entrada 1

```
t = linspace(0,2.5,1000);
```

```
u = u0 + 1*esc(t,0.1) - 1*ram(t,1) + 1*ram(t,1.5);
```

% Simulación 1

```
[~,~,x_l] = lsim(iman_lineal, u-u0,t,[0 0 0]);
```

```
[~,x_nl] = ode45(@iman_no_lineal,t,[x10 x20 x30]);
```

```
figure
```

```
subplot(411), plot(t,u,'b'), axis tight, ylabel('Voltaje (V)'), legend('\itu(t)','Location','eastoutside')
```


```
subplot(412), plot(t,x_nl(:,1)*100,'g',t,(x_l(:,1)+x10)*100,'--'), axis tight, ylabel('Posición (cm)'),
```

```
legend('\itx_1^{nl}(t)','\itx_1^{l}(t)','Location','eastoutside')
```

```
subplot(413), plot(t,x_nl(:,2)*100,'k',t,(x_l(:,2)+x20)*100,'--'), axis tight, ylabel('Velocidad (cm/s)'),
```


```
legend('\itx_2^{nl}(t)','\itx_2^{l}(t)','Location','eastoutside')
```
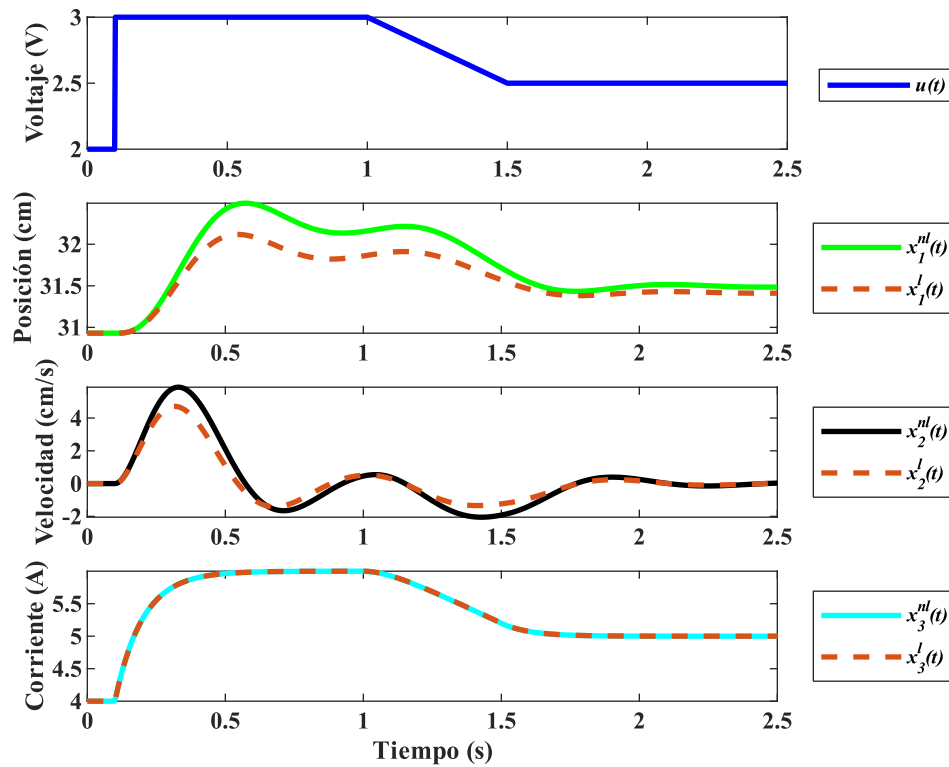
```
subplot(414), plot(t,x_nl(:,3),'c',t,x_l(:,3)+x30,'--'), axis tight, ylabel('Corriente (A)'), legend('\itx_3^{nl}(t)','\itx_3^{l}(t)','Location','eastoutside'), xlabel('Tiempo (s)')
```



```
% Entrada 2
t = linspace(0,2.5,1000);
u = u0 - 2*ram(t,0.2) + 2*ram(t,1.2) + 5*esc(t,1.5);
% Simulación 2
[~,~,x_l] = lsim(iman_lineal, u-u0,t,[0 0 0]);
[~,x_nl] = ode45(@iman_no_lineal2,t,[x10 x20 x30]);
figure
subplot(411), plot(t,u,'b'), axis tight, ylabel('Voltaje (V)'), legend('\itu(t)', 'Location', 'eastoutside')
subplot(412), plot(t,x_nl(:,1)*100,'g',t,(x_l(:,1)+x10)*100,'--'), axis tight, ylabel('Posición (cm)'),
legend('\itx_1^{nl}(t)', '\itx_1^{l}(t)', 'Location', 'eastoutside')
subplot(413), plot(t,x_nl(:,2)*100,'k',t,(x_l(:,2)+x20)*100,'--'), axis tight, ylabel('Velocidad (cm/s)'),
legend('\itx_2^{nl}(t)', '\itx_2^{l}(t)', 'Location', 'eastoutside')
```
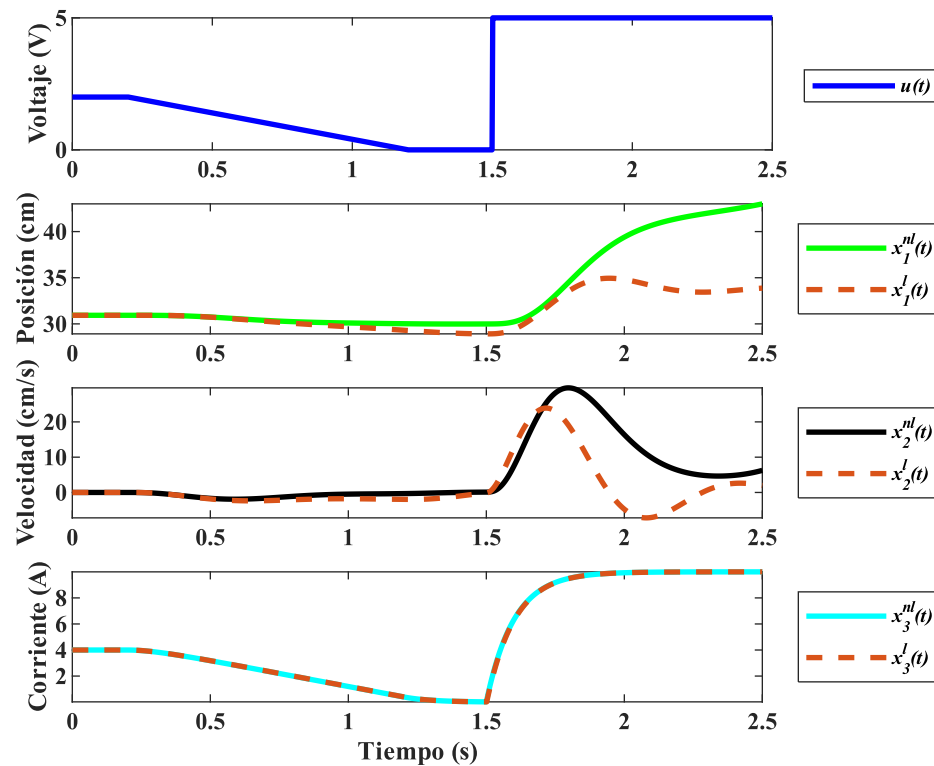
```
subplot(414), plot(t,x_n1(:,3),'c',t,x_l(:,3)+x30,'--'), axis tight, ylabel('Corriente (A)'), legend('\itx_3^{nl}(t)', '\itx_3^{l}(t)', 'Location', 'eastoutside'), xlabel('Tiempo (s)')
```



% Entrada 3

```
t = linspace(0,2.5,1000);
```

```
u = u0 + 10*ram(t,0.1) - 10*ram(t,0.6) - 5*esc(t,0.6) + 8*sin(2*pi*3*t).*esc(t,1.25);
```

% Simulación 3

```
[~,~,x_l] = lsim(iman_lineal, u-u0,t,[0 0 0]);
```

```
[~,x_n1] = ode45(@iman_no_lineal3,t,[x10 x20 x30]);
```

```
figure
```


```
subplot(411), plot(t,u,'b'), axis tight, ylabel('Voltaje (V)'), legend('\itu(t)', 'Location', 'eastoutside')
```

```
subplot(412), plot(t,x_n1(:,1)*100,'g',t,(x_l(:,1)+x10)*100,'--'), axis tight, ylabel('Posición (cm)'),
```

```
legend('\itx_1^{nl}(t)', '\itx_1^{l}(t)', 'Location', 'eastoutside')
```


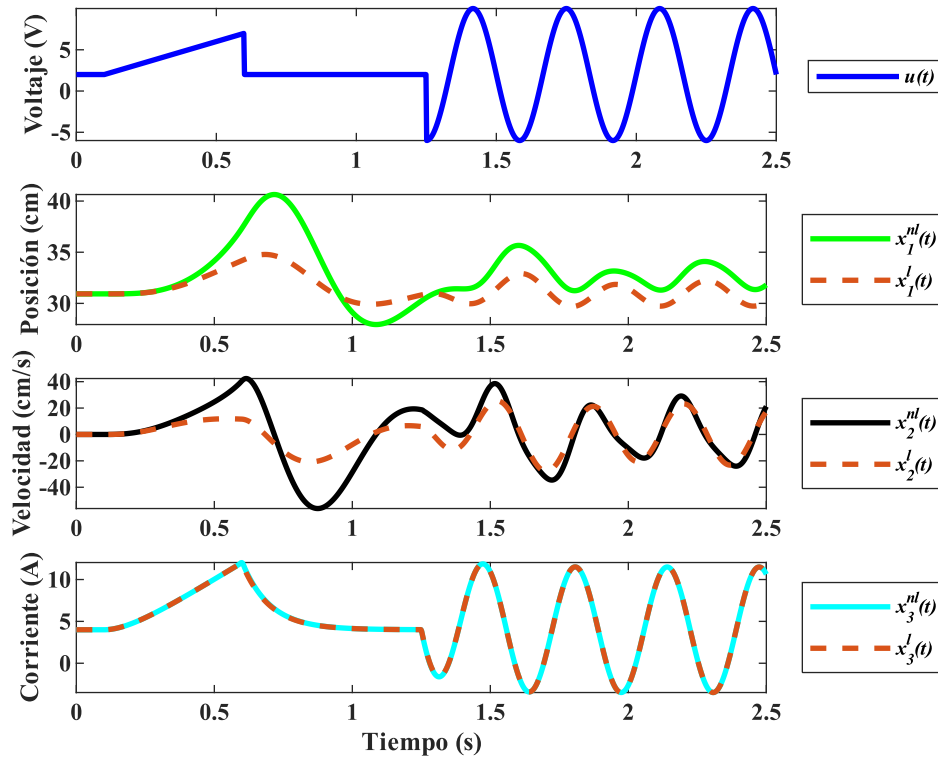
```
subplot(413), plot(t,x_n1(:,2)*100,'k',t,(x_l(:,2)+x20)*100,'--'), axis tight, ylabel('Velocidad (cm/s)'),
legend('\itx_2^{nl}(t)', '\itx_2^{l}(t)', 'Location', 'eastoutside')
subplot(414), plot(t,x_n1(:,3), 'c', t, x_l(:,3)+x30, '--'), axis tight, ylabel('Corriente (A)'), legend('\itx_3^{nl}
(t)', '\itx_3^{l}(t)', 'Location', 'eastoutside'), xlabel('Tiempo (s)')
```



e) Reducción de orden.

La dinámica de la corriente se asume instantanea. Se reduce en 1 el orden y la cantidad de variables de estado.

$$\frac{d}{dt}x_3(t) = \frac{1}{L}u(t) - \frac{R}{L}x_3(t) = 0$$

$$x_3(t) = \frac{1}{R}u(t)$$


Modelo.

$$\frac{d}{dt}x_1(t) = x_2(t),$$

$$\frac{d}{dt}x_2(t) = \frac{1}{M} \frac{k_i \left(\frac{1}{R} u(t) \right)^2}{l_1 - x_1(t) + a} - \frac{k}{M} (x_1(t) - l_0) - \frac{d}{M} x_2(t).$$


Simulación.

```
% Entrada 1
t = linspace(0,2.5,1000);
u = u0 + 1*esc(t,0.1) - 1*ram(t,1) + 1*ram(t,1.5);
% Simulación 1
[~,~,x_l] = lsim(iman_lineal, u-u0,t,[0 0 0]);
[~,x_nl] = ode45(@iman_no_lineal,t,[x10 x20 x30]);
[~,x_nl_r] = ode45(@iman_no_lineal_reducido,t,[x10 x20]);
figure
subplot(411), plot(t,u,'b'), axis tight, ylabel('Voltaje (V)'), legend('\itu(t)', 'Location', 'eastoutside')
subplot(412), plot(t,x_nl(:,1)*100,'g',t,(x_l(:,1)+x10)*100,'--',t,x_nl_r(:,1)*100,':'), axis tight,
ylabel('Posición (cm)'), legend('\itx_1^{nl}(t)', '\itx_1^{l}(t)', '\itx_1^{nlr}(t)', 'Location', 'eastoutside')
subplot(413), plot(t,x_nl(:,2)*100,'k',t,(x_l(:,2)+x20)*100,'--',t,x_nl_r(:,2)*100,':'), axis tight,
ylabel('Velocidad (cm/s)'), legend('\itx_2^{nl}(t)', '\itx_2^{l}(t)', '\itx_2^{nlr}(t)', 'Location', 'eastoutside')
subplot(414), plot(t,x_nl(:,3),'c',t,x_l(:,3)+x30,'--',t,u/R,':'), axis tight, ylabel('Corriente (A)'),
legend('\itx_3^{nl}(t)', '\itx_3^{l}(t)', '\itx_3^{nlr}(t)', 'Location', 'eastoutside'), xlabel('Tiempo (s)')
```

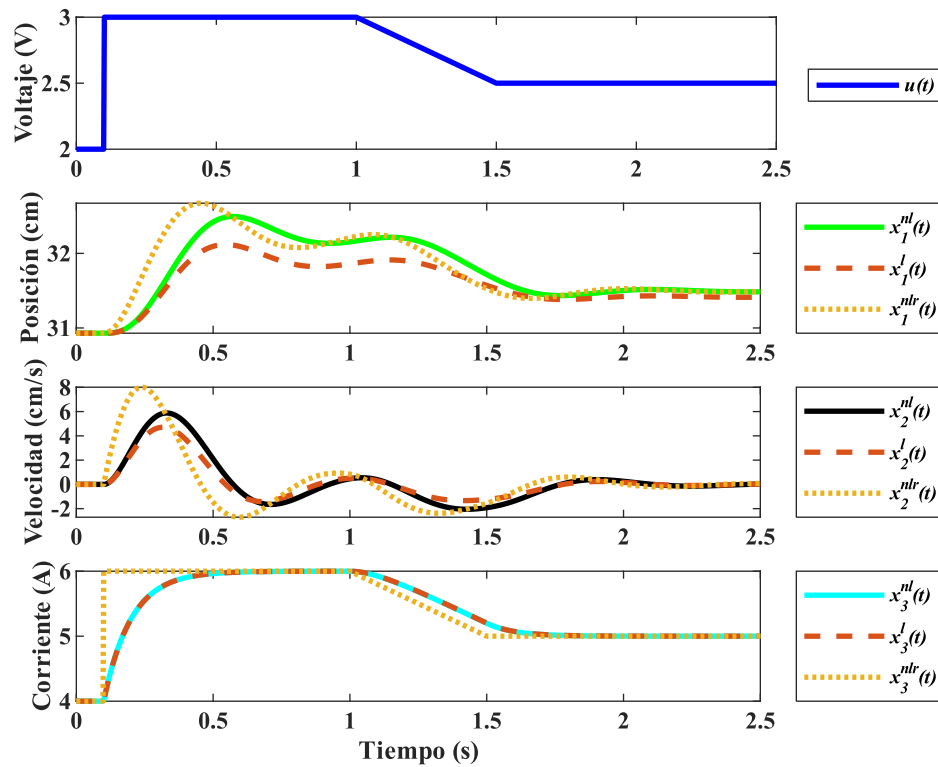

```
% Entrada 2
t = linspace(0,2.5,1000);
u = u0 - 2*ram(t,0.2) + 2*ram(t,1.2) + 5*esc(t,1.5);
% Simulación 2
[~,~,x_l] = lsim(iman_lineal, u-u0,t,[0 0 0]);
[~,x_nl] = ode45(@iman_no_lineal2,t,[x10 x20 x30]);
[~,x_nl_r] = ode45(@iman_no_lineal2_reducido,t,[x10 x20]);
figure
subplot(411), plot(t,u,'b'), axis tight, ylabel('Voltaje (V)'), legend('\itu(t)', 'Location', 'eastoutside')
subplot(412), plot(t,x_nl(:,1)*100,'g',t,(x_l(:,1)+x10)*100,'--',t,x_nl_r(:,1)*100,':'), axis tight,
ylabel('Posición (cm)'), legend('\itx_1^{nl}(t)', '\itx_1^l(t)', '\itx_1^{nlr}(t)', 'Location', 'eastoutside')
subplot(413), plot(t,x_nl(:,2)*100,'k',t,(x_l(:,2)+x20)*100,'--',t,x_nl_r(:,2)*100,':'), axis tight,
ylabel('Velocidad (cm/s)'), legend('\itx_2^{nl}(t)', '\itx_2^l(t)', '\itx_2^{nlr}(t)', 'Location', 'eastoutside')
```
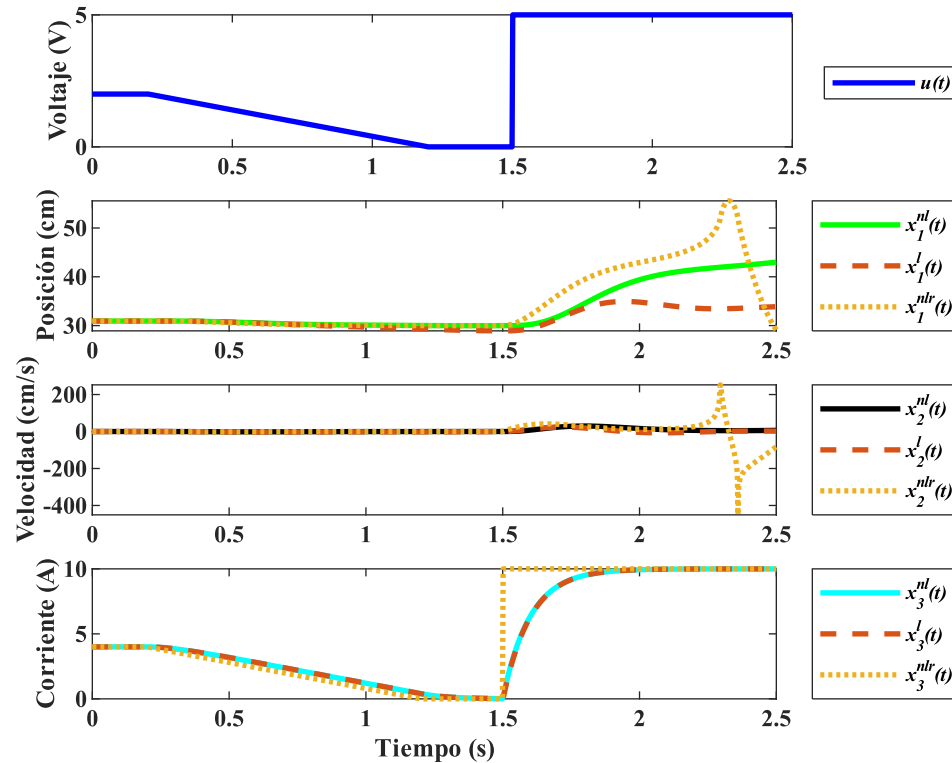
```
subplot(414), plot(t,x_n1(:,3),'c',t,x_l(:,3)+x30,'--',t,u/R,':'), axis tight, ylabel('Corriente (A)'),
legend('\itx_3^{nl}(t)', '\itx_3^{l}(t)', '\itx_3^{nlr}(t)', 'Location', 'eastoutside'), xlabel('Tiempo (s)')
```




```
% Entrada 3
t = linspace(0,2.5,1000);
u = u0 + 10*ram(t,0.1) - 10*ram(t,0.6) - 5*esc(t,0.6) + 8*sin(2*pi*3*t).*esc(t,1.25);
% Simulación 3
[~,~,x_l] = lsim(iman_lineal, u-u0,t,[0 0 0]);
[~,x_n1] = ode45(@iman_no_lineal3,t,[x10 x20 x30]);
[~,x_n1_r] = ode45(@iman_no_lineal3_reducido,t,[x10 x20]);
figure
subplot(411), plot(t,u,'b'), axis tight, ylabel('Voltaje (V)'), legend('\itu(t)', 'Location', 'eastoutside')
subplot(412), plot(t,x_n1(:,1)*100,'g',t,(x_l(:,1)+x10)*100,'--',t,x_n1_r(:,1)*100,':'), axis tight,
ylabel('Posición (cm)'), legend('\itx_1^{nl}(t)', '\itx_1^{l}(t)', '\itx_1^{nlr}(t)', 'Location', 'eastoutside')
```

```

subplot(413), plot(t,x_n1(:,2)*100,'k',t,(x_l(:,2)+x20)*100,'--',t,x_n1_r(:,2)*100,':'), axis tight,
ylabel('Velocidad (cm/s)'), legend('\itx_2^{nl}(t)', '\itx_2^{l}(t)', '\itx_2^{nlr}(t)', 'Location', 'eastoutside')
subplot(414), plot(t,x_n1(:,3), 'c', t, x_l(:,3)+x30, '--', t, u/R, ':'), axis tight, ylabel('Corriente (A)'),
legend('\itx_3^{nl}(t)', '\itx_3^{l}(t)', '\itx_3^{nlr}(t)', 'Location', 'eastoutside'), xlabel('Tiempo (s)')

```

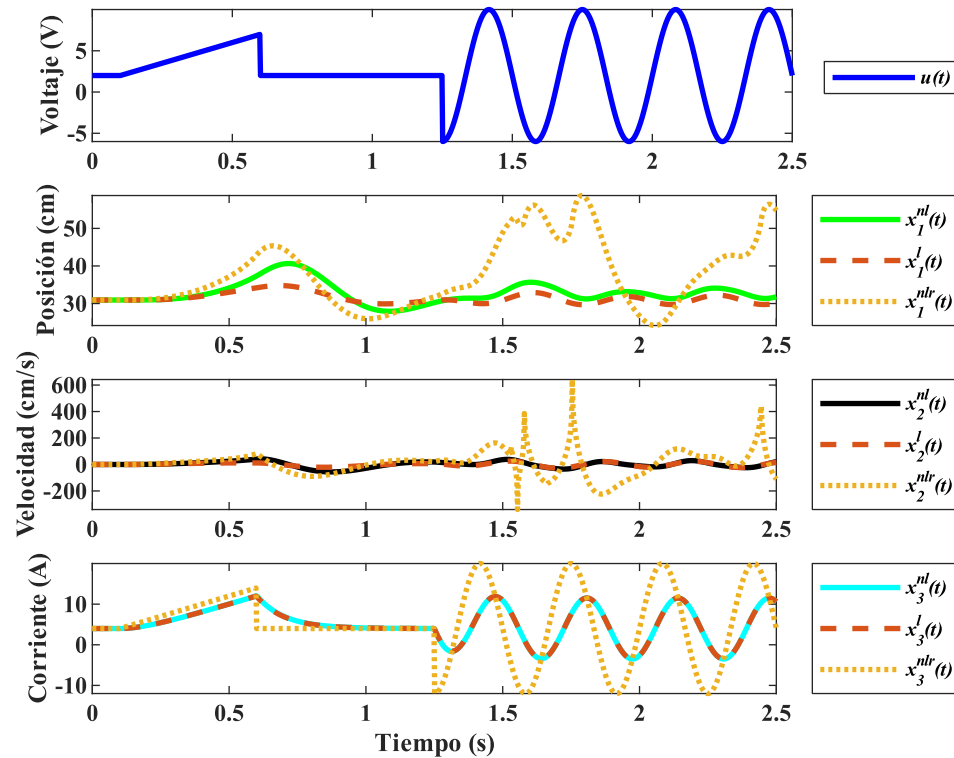

Problema 2: Estudiar circuito RLC discreto.

Sistema.

```

A = [0.775 8.327; -0.042 0.609]; B = [0.225 0.042]'; C = [1 0]; D = 0;
T = 0.02;
RLC = ss(A,B,C,D,T)

```

RLC =

A =

	x1	x2
x1	0.775	8.327
x2	-0.042	0.609

B =

	u1
x1	0.225
x2	0.042

C =

	x1	x2
y1	1	0


D =

	u1
y1	0

Sample time: 0.02 seconds
Discrete-time state-space model.
Model Properties

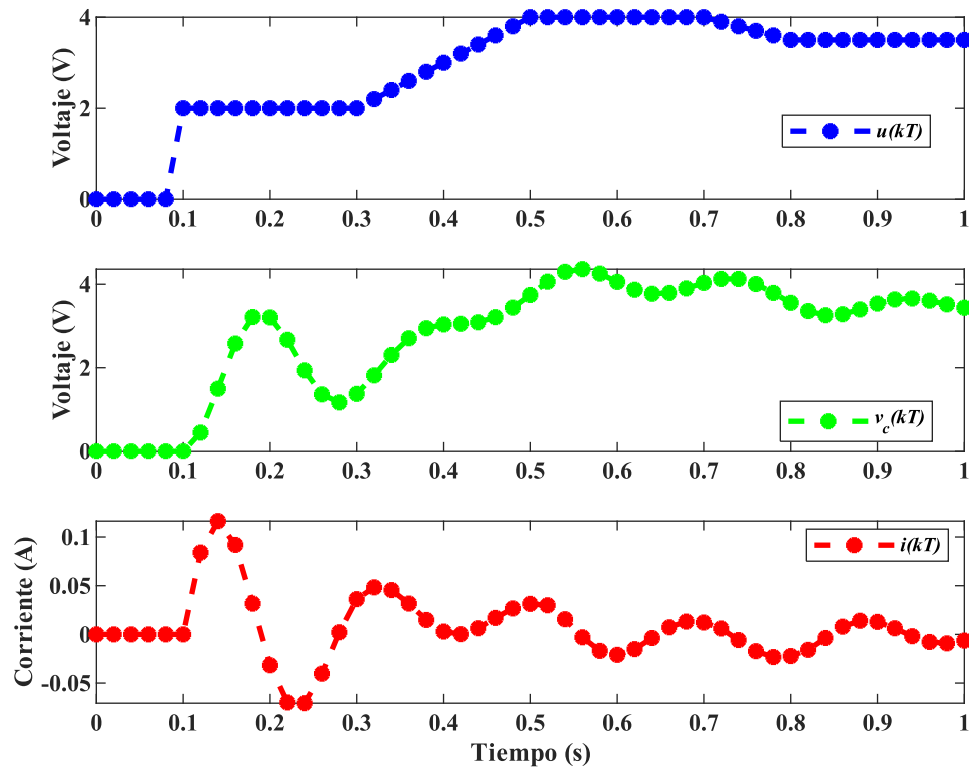
a) Simulación

```
k = 0:50;  
kT = k*T;  
e = 2*esc(kT,5*T) + 10*ram(kT,15*T) - 10*ram(kT,25*T) - 5*ram(kT,35*T) + 5*ram(kT,40*T);  
[~,~,x] = lsim(RLC,e,kT);  
figure  
subplot(311),plot(kT,e,'b--*'), axis tight, ylabel('Voltaje (V)'), legend('\itu(kT)','Location','best')  
subplot(312),plot(kT,x(:,1),'g--*'), axis tight, ylabel('Voltaje (V)'), legend('\itv_c(kT)','Location','best')  
subplot(313),plot(kT,x(:,2),'r--*'), axis tight, ylabel('Corriente (A)'), legend('\iti(kT)','Location','best'),  
xlabel('Tiempo (s)')
```




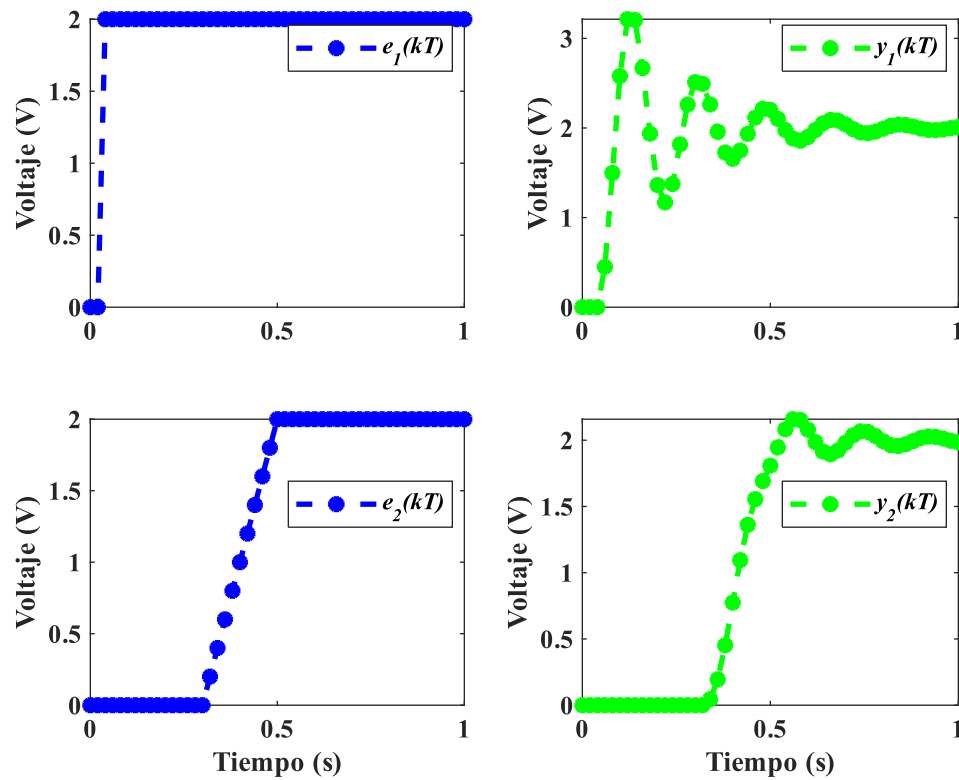b) Principio de superposición y homogeneidad.

```
e1 = 2*esc(kT,2*T); [y1,~,~] = lsim(RLC,e1,kT);
e2 = 10*ram(kT,15*T) - 10*ram(kT,25*T); [y2,~,~] = lsim(RLC,e2,kT);
figure
subplot(221), plot(kT,e1,'b--*'), axis tight, ylabel('Voltaje (V)'), legend('\ite_1(kT)','Location','best')
subplot(222), plot(kT,y1,'g--*'), axis tight, ylabel('Voltaje (V)'), legend('\ity_1(kT)','Location','best')
subplot(223), plot(kT,e2,'b--*'), axis tight, ylabel('Voltaje (V)'), legend('\ite_2(kT)','Location','best'),
xlabel('Tiempo (s)')
subplot(224), plot(kT,y2,'g--*'), axis tight, ylabel('Voltaje (V)'), legend('\ity_2(kT)','Location','best'),
xlabel('Tiempo (s)')
```




```
[y1_2,~,~] = lsim(RLC,e1+e2,kT);
alpha = 3;
[alpha_y1,~,~] = lsim(RLC,alpha*e1,kT);
figure
subplot(211),plot(kT,y1_2,'g--*',kT,y1+y2,'mo'), axis tight, ylabel('Voltaje (V)'), legend('\itH(e_1(kT)
+e_2(kT))', '\ity_1(kT)+y_2(kT)', 'Location', 'best')
subplot(212),plot(kT,alpha_y1,'g--*',kT,alpha*y1,'mo'), axis tight, ylabel('Voltaje (V)'),
legend('\itH(\alpha e_1(kT))', '\itay_1(kT)', 'Location', 'best'), xlabel('Tiempo (s)')
```

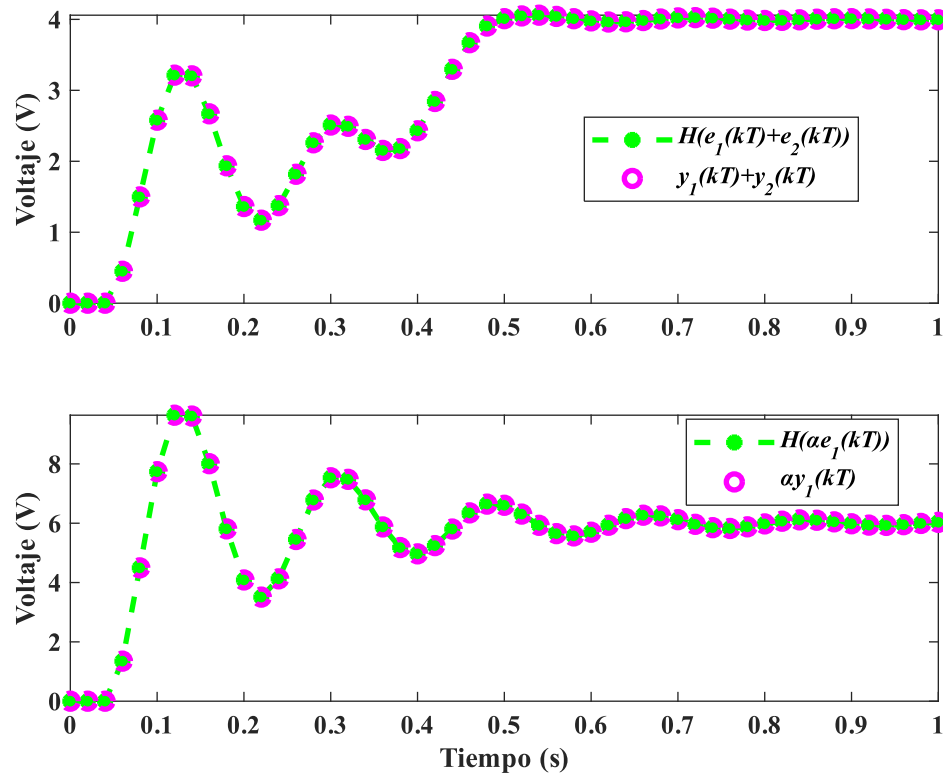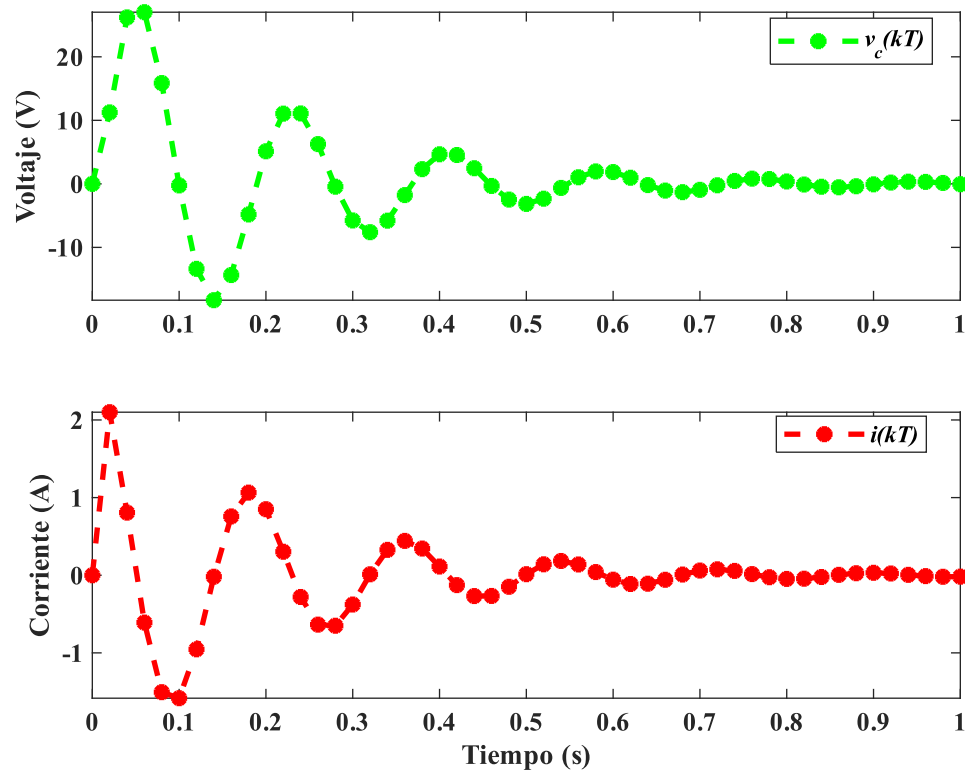
c) Respuesta a entrada discreta impulso.

```
[~,~,x] = impulse(RLC,kT);
figure
subplot(211),plot(kT,x(:,1),'g--*'), axis tight, ylabel('Voltaje (V)'), legend('\itv_c(kT)','Location','best')
subplot(212),plot(kT,x(:,2),'r--*'), axis tight, ylabel('Corriente (A)'), legend('\iti(kT)','Location','best'),
xlabel('Tiempo (s)')
```




Respuesta a entrada escalón.
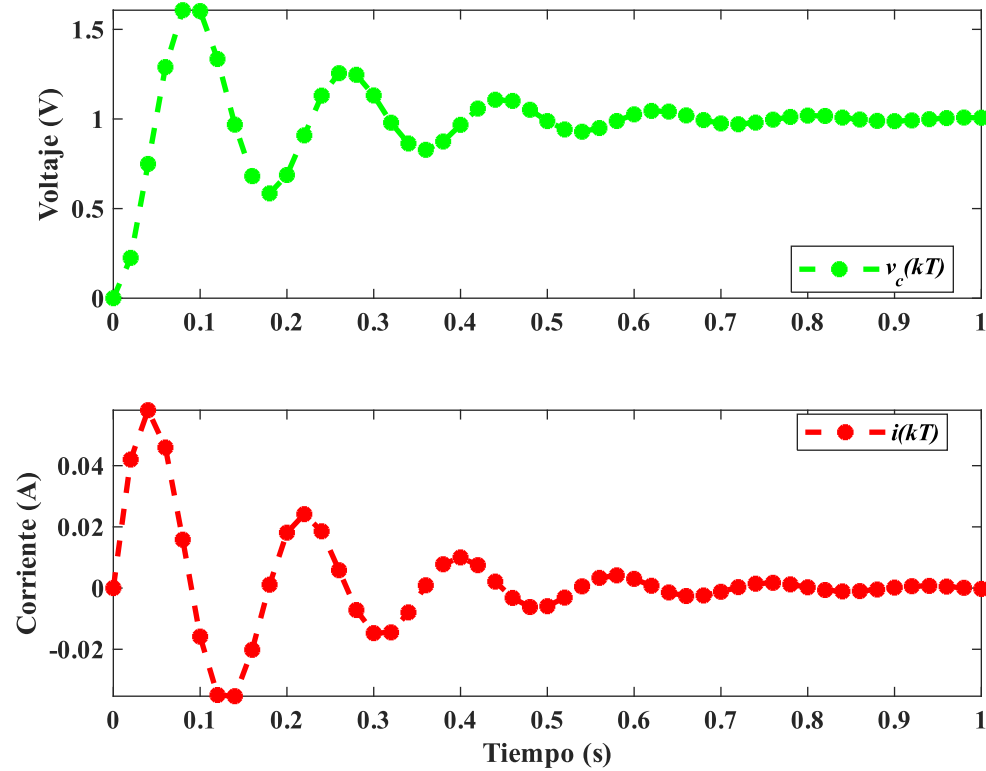
```
[~,~,x] = step(RLC,kT);
figure
subplot(211),plot(kT,x(:,1),'g--*'), axis tight, ylabel('Voltaje (V)'), legend('\itv_c(kT)','Location','best')
subplot(212),plot(kT,x(:,2),'r--*'), axis tight, ylabel('Corriente (A)'), legend('\iti(kT)','Location','best'),
xlabel('Tiempo (s)')
```



Respuesta a entrada rampa.

```
u = ram(kT,0);
[~,~,x] = lsim(RLC,u,kT);
figure
subplot(211),plot(kT,x(:,1),'g--*'), axis tight, ylabel('Voltaje (V)'), legend('\itv_c(kT)','Location','best')
subplot(212),plot(kT,x(:,2),'r--*'), axis tight, ylabel('Corriente (A)'), legend('\iti(kT)','Location','best'),
xlabel('Tiempo (s)')
```

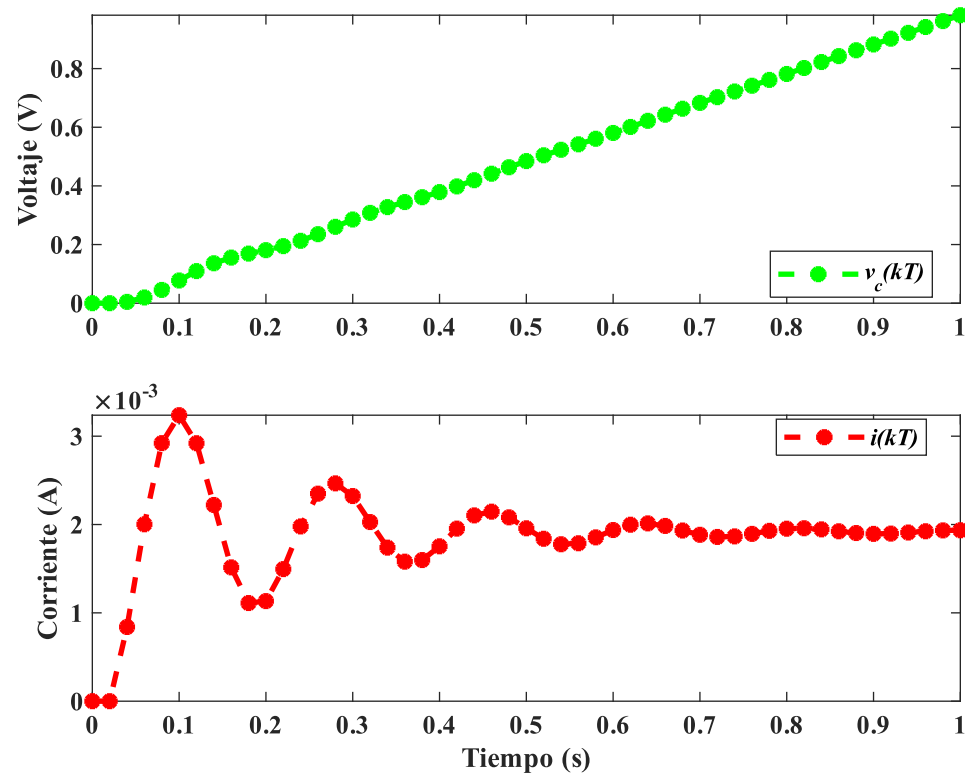

Problema 3: Preguntas de desarrollo.

a) Respuesta de un S.L.I. ante entrada arbitraria.


$$h(t) = \frac{d}{dt} y_{\text{step}}(t) = e^{-\frac{t}{2}} u(t)$$

$$y(t) = e^{-\frac{t-2}{2}} u(t-2) - 2 \left(1 - e^{-\frac{t-4}{2}} \right) u(t-4)$$

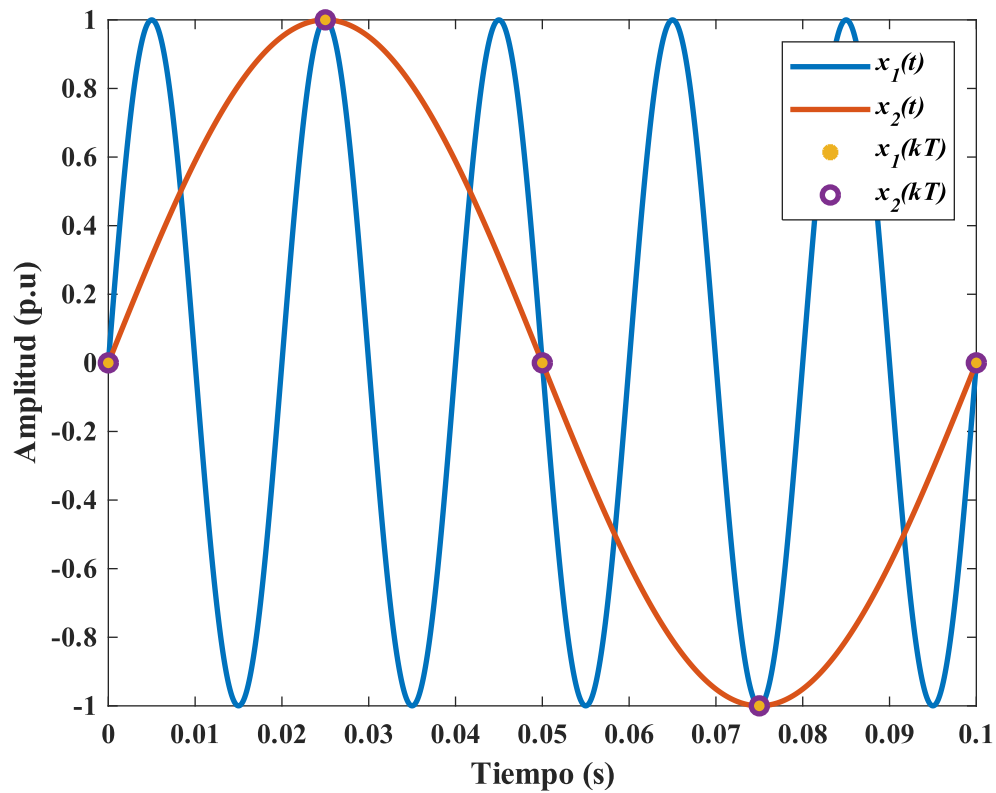b) Aliasing.

Dos señales tiempo continuo son indistinguibles en tiempo discreto debido a un muestreo insuficiente.

```
f1 = 50;  
f2 = 10;  
ts = 0.025;  
Tend = 1/f2;  
kT = 0:ts:Tend;  
t = linspace(0,Tend,1000);  
x1 = sin(2*pi*f1*kT);  
x2 = sin(2*pi*f2*kT);  
figure()  
plot(t,sin(2*pi*f1*t),t,sin(2*pi*f2*t),kT,x1,'*',kT,x2,'o'),  
legend('\itx_1(t)', '\itx_2(t)', '\itx_1(kT)', '\itx_2(kT)'), xlabel('Tiempo (s)'), ylabel('Amplitud (p.u)')
```



c) Transformada de Laplace.

```
syms t
f1 = 2/3*(t+3)*heaviside(t+3) - 4/3*t*heaviside(t) + 2/3*(t-3)*heaviside(t-3);
f1_s = laplace(f1)
```

f1_s =

$$\frac{2(3s+1)}{3s^2} + \frac{2e^{-3s}}{3s^2} - \frac{4}{3s^2}$$

```
f2 = -heaviside(t+2) + 2*heaviside(t) - heaviside(t-2);
f2_s = laplace(f2)
```

f2_s =

$$\frac{1}{s} - \frac{e^{-2s}}{s}$$

```
function dx = iman_no_lineal(t,x) % Definición del imán no lineal para entrada 1.
% Parametros
R = 0.5;
L = 50e-3;
a = 2e-2;
ki = 3e-3;
l1 = 50e-2;
l0 = 30e-2;
M = 250e-3;
k = 24.5;
d = 1.5;
% Entrada
u0 = 2;%3542/765;
u = u0 + 1*esc(t,0.1) - 1*ram(t,1) + 1*ram(t,1.5);
% Ecuaciones diferenciales
dx(1) = x(2);
dx(2) = (1/M)*ki*x(3)*x(3)/(l1 - x(1) + a) - k/M*(x(1) - l0) - d/M*x(2);
dx(3) = 1/L*u - R/L*x(3);
dx = [dx(1); dx(2); dx(3)];
```

```

end
function dx = iman_no_lineal2(t,x) % Definición del imán no lineal para entrada 2.
% Parametros
R = 0.5;
L = 50e-3;
a = 2e-2;
ki = 3e-3;
l1 = 50e-2;
l0 = 30e-2;
M = 250e-3;
k = 24.5;
d = 1.5;
% Entrada
u0 = 2;%3542/765;
u = u0 - 2*ram(t,0.2) + 2*ram(t,1.2) + 5*esc(t,1.5);
% Ecuaciones diferenciales
dx(1) = x(2);
dx(2) = (1/M)*ki*x(3)*x(3)/(l1 - x(1) + a) - k/M*(x(1) - l0) - d/M*x(2);
dx(3) = 1/L*u - R/L*x(3);
dx = [dx(1); dx(2); dx(3)];
end
function dx = iman_no_lineal3(t,x) % Definición del imán no lineal para entrada 3.
% Parametros
R = 0.5;
L = 50e-3;
a = 2e-2;
ki = 3e-3;
l1 = 50e-2;
l0 = 30e-2;
M = 250e-3;
k = 24.5;
d = 1.5;
% Entrada
u0 = 2;%3542/765;
u = u0 + 10*ram(t,0.1) - 10*ram(t,0.6) - 5*esc(t,0.6) + 8*sin(2*pi*3*t).*esc(t,1.25);
% Ecuaciones diferenciales
dx(1) = x(2);

```

```

dx(2) = (1/M)*ki*x(3)*x(3)/(l1 - x(1) + a) - k/M*(x(1) - l0) - d/M*x(2);
dx(3) = 1/L*u - R/L*x(3);
dx = [dx(1); dx(2); dx(3)];
end
function dx = iman_no_lineal_reducido(t,x) % Definición del imán no lineal reducido para entrada 1.
% Parametros
R = 0.5;
L = 50e-3;
a = 2e-2;
ki = 3e-3;
l1 = 50e-2;
l0 = 30e-2;
M = 250e-3;
k = 24.5;
d = 1.5;
% Entrada
u0 = 2;%3542/765;
u = u0 + 1*esc(t,0.1) - 1*ram(t,1) + 1*ram(t,1.5);
% Ecuaciones diferenciales
i = u/R;
dx(1) = x(2);
dx(2) = (1/M)*ki*i^2/(l1 - x(1) + a) - k/M*(x(1) - l0) - d/M*x(2);
dx = [dx(1); dx(2)];
end
function dx = iman_no_lineal2_reducido(t,x) % Definición del imán no lineal reducido para entrada 2.
% Parametros
R = 0.5;
L = 50e-3;
a = 2e-2;
ki = 3e-3;
l1 = 50e-2;
l0 = 30e-2;
M = 250e-3;
k = 24.5;
d = 1.5;
% Entrada
u0 = 2;%3542/765;

```



```

u = u0 - 2*ram(t,0.2) + 2*ram(t,1.2) + 5*esc(t,1.5);
% Ecuaciones diferenciales
i = u/R;
dx(1) = x(2);
dx(2) = (1/M)*ki*i^2/(l1 - x(1) + a) - k/M*(x(1) - l0) - d/M*x(2);
dx = [dx(1); dx(2)];
end
function dx = iman_no_lineal3_reducido(t,x) % Definición del imán no lineal reducido para entrada 3.
% Parametros
R = 0.5;
L = 50e-3;
a = 2e-2;
ki = 3e-3;
l1 = 50e-2;
l0 = 30e-2;
M = 250e-3;
k = 24.5;
d = 1.5;
% Entrada
u0 = 2;%3542/765;
u = u0 + 10*ram(t,0.1) - 10*ram(t,0.6) - 5*esc(t,0.6) + 8*sin(2*pi*3*t).*esc(t,1.25);
% Ecuaciones diferenciales
i = u/R;
dx(1) = x(2);
dx(2) = (1/M)*ki*i^2/(l1 - x(1) + a) - k/M*(x(1) - l0) - d/M*x(2);
dx = [dx(1); dx(2)];
end
function u = esc(t,t0)
    u = t>=t0;
end
function r = ram(t,t0)
    r = (t - t0).*esc(t,t0);
end

```